




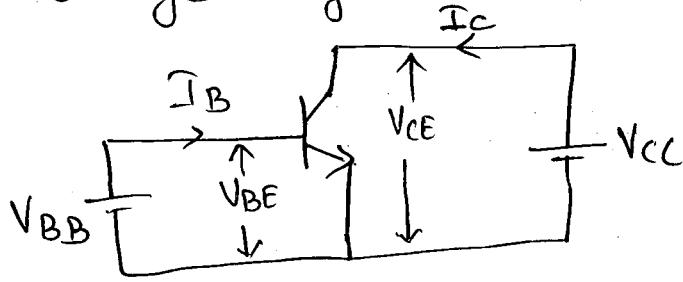
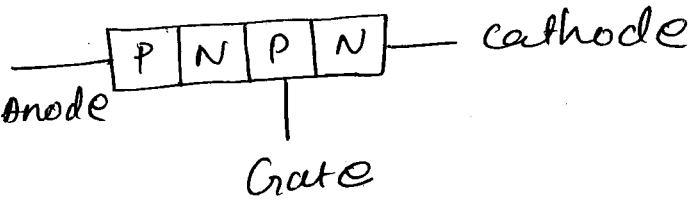
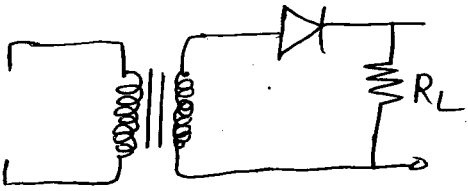
1/4


ANSWER KEYIMPROVEMENT October  
FIRST YEAR HIGHER SECONDARY EXAMINATION MARCH 2022




PART-I/II/III

SUBJECT: ELECTRONICSCODE NO: FY831VERSION: D60 SCORES2 HOURS

Qn. No	Sub Qns	Answer Key/Value Points	Score	Total Score
1			1	1
2		Ampere (ആംപിയർ)	1	1
3		1.1 eV	1	1
4			1	1
5		photo diode	1	1
6		1.21	1	1
7		voltage divider biasing circuit	1	1
8		.7V	1	1
9		3	1	1
10		2	1	1
11		$22 \times 10^2 \Omega \pm 5\%$ OR $2.2 \text{ k}\Omega \pm 5\%$	2	2
12		There is no free carriers in semiconductor at absolute zero temperature	2	2

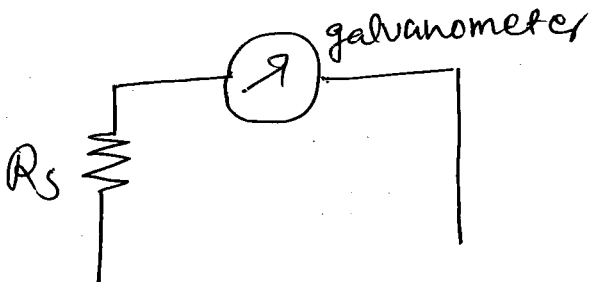Qn. No	Sub Qns	Answer Key/Value Points	Score	Total Score
13	a.		1	2
	b.	voltage regulator	1	
14.			2	2
15.			2	2
16.		Any two differences	1+1	2
17.			2	2
18.		$A\beta = 1$	1	2
		$\angle A\beta = 0^\circ \text{ or } 360^\circ$	1	
19.		Diagram of damped and unclamped oscillations	1+1	2
20.		$C = \frac{\epsilon A}{d}$	1	3
		Area of conducting plates } Any distance between plates } two permittivity of dielectric }	2	

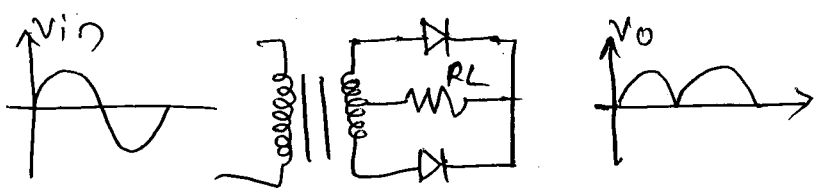Qn. No	Sub Qns	Answer Key/Value Points	Score	Total Score
21		Explanation		
	a	cycle	1	3
	b	Time period	1	
	c	frequency	1	
22		Energy band diagrams of insulator, semiconductor & conductor.	3	3
23.		forward characteristics reverse characteristics	$1\frac{1}{2}$ $1\frac{1}{2}$	3
24		6 steps $6 \times \frac{1}{2} = 3$	3	3
25		3 comparisons size, doping and carrier movement.	3	3
26.		circuit diagram	3	3
27.		$(101 \cdot 11)_2 = (5 \cdot 75)_{10}$	3	3
28.		circuit diagram $A = -\frac{R_2}{R_1}$	2 1	3
29.	a).	large value resistor	1	3
	b)		2	

Qn. No	Sub Qns	Answer Key/Value Points	Score	Total Score															
30		Total resistance = $10\Omega$ Total current = $10/10 = 1A$ Current through $5\Omega = 1A$ Current through $10\Omega = 0.5A$	1 1 1 1	4															
31		CE input characteristics output characteristics	2 2	4															
32			1+2+1	4															
33		Circuit diagram $f = \frac{1}{2\pi\sqrt{LC}}$	3 1	4															
34		 <table border="1" data-bbox="766 1108 981 1321"> <thead> <tr> <th>A</th> <th>B</th> <th>Y</th> </tr> </thead> <tbody> <tr> <td>0</td> <td>0</td> <td>0</td> </tr> <tr> <td>0</td> <td>1</td> <td>1</td> </tr> <tr> <td>1</td> <td>0</td> <td>1</td> </tr> <tr> <td>1</td> <td>1</td> <td>1</td> </tr> </tbody> </table>	A	B	Y	0	0	0	0	1	1	1	0	1	1	1	1	2+2	4
A	B	Y																	
0	0	0																	
0	1	1																	
1	0	1																	
1	1	1																	
35	a)	$R = R_1 + R_2 + R_3 = 9 + 9 + 9 = 27\Omega$	2	4															
	b)	$\frac{1}{R} = \frac{1}{9} + \frac{1}{9} + \frac{1}{9} = \frac{3}{9} \therefore R = \frac{9}{3} = 3\Omega$	2																
36	a)	$V_{rms} = \frac{V_m}{\sqrt{2}} = \frac{10}{\sqrt{2}} = 7.07V$	1	4															
	b)	$V_{dc} = \frac{2V_m}{\pi} = \frac{2 \times 10}{3.14} = 6.37V$	1																
	c)	ripple factor $r = \sqrt{\left(\frac{V_{rms}}{V_{dc}}\right)^2 - 1} = 0.48$	2																
37	a)	$(16)_{10} = (10000)_2$	1	4															
	b)	 <table border="1" data-bbox="774 1937 957 2139"> <thead> <tr> <th>A</th> <th>B</th> <th>Y</th> </tr> </thead> <tbody> <tr> <td>0</td> <td>0</td> <td>0</td> </tr> <tr> <td>0</td> <td>1</td> <td>0</td> </tr> <tr> <td>1</td> <td>0</td> <td>0</td> </tr> <tr> <td>1</td> <td>1</td> <td>1</td> </tr> </tbody> </table>	A		B	Y	0	0	0	0	1	0	1	0	0	1	1	1	$1\frac{1}{2} + 1\frac{1}{2} = 3$
A	B	Y																	
0	0	0																	
0	1	0																	
1	0	0																	
1	1	1																	